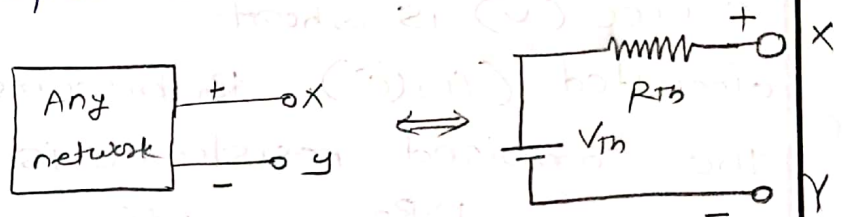


* Thevenin's Theorem:-

Thevenin theorem states that the entire network connected to two terminals can be replaced by a single voltage source V_{th} in series with single resistance R_{th} connected to same the two terminals.


V_{th} is open circuit voltage across terminals x & y . R_{th} is open circuit resistance across x & y .



Any network converted to the Thevenin equivalent circuit.


Consider an example. (fig @). Let us find the voltage V_L & current I_L through load resistance R_L of 2Ω .

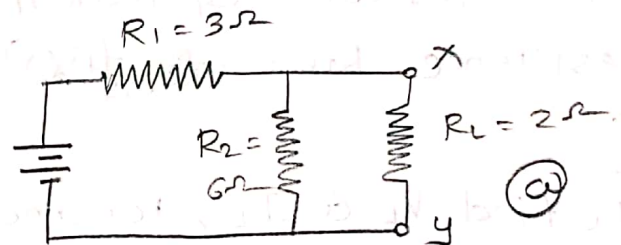Step 1 (a) original circuit with load resistance $V=36V$ R_L across x & y



Step 2 (b) To apply Thevenin theorem, disconnected R_L in fig (b)

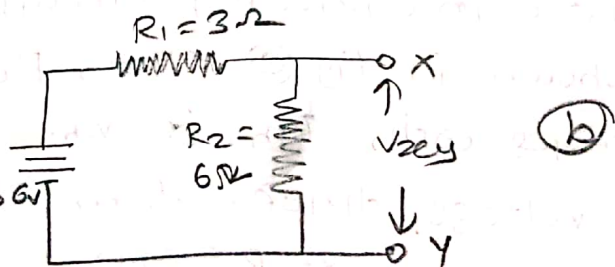As a result, $R_1 = 3\Omega$ & $R_2 = 6\Omega$ form a series voltage $V=36V$ divider. Now,




voltage across R_2 is same as open circuit voltage V_{xy} . Using voltage divider formula,

$$V_{R_2} = \frac{R_2}{R_1 + R_2} \times V = \frac{6}{3+6} \times 36 = \frac{6}{9} \times 36$$

$$\therefore V_{R_2} = 24V = V_{oc}$$

This is V_{th} . It is positive at terminal x.

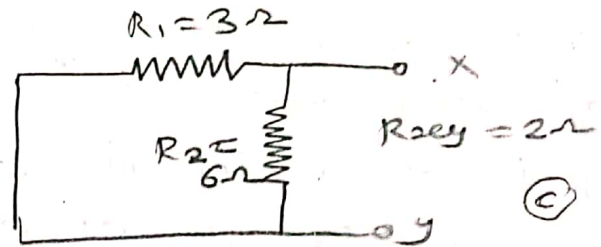Step 3:- To find R_{th} , load resistance R_L is still disconnected. Now, source (V) is short




circuit (fig c). R_1 becomes parallel to R_2 . The combined resistance is,

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$


Step 4:-

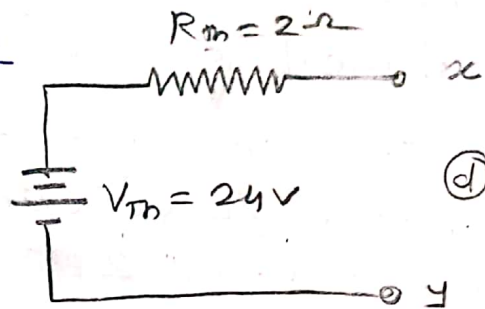Hence thevenin equivalent circuit consists of equivalent voltage $V_{th} = 24V$ in series with equivalent resistance $R_{th} = 2\Omega$ (fig d).



Step 5:-

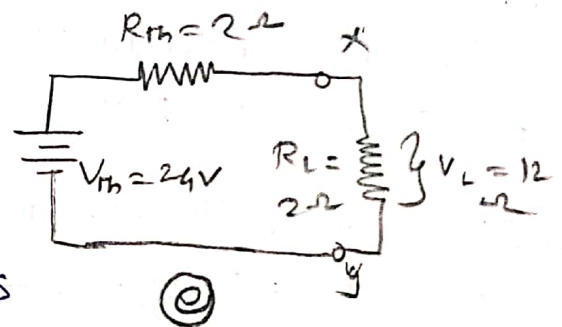To find V_L & I_L , reconnect R_L to terminals x & y of Thevenin equivalent circuit as shown in fig e. Then R_L is in series with R_{th} & V_{th} .



Using voltage divider formula for $R_{th} = 2\Omega$ & $R_L = 2\Omega$

$$V_L = \frac{R_L}{R_{th} + R_L} \times V_{th} = \frac{2}{4} \times 24 = 12V$$

$$I_L = \frac{V_L}{R_L} = \frac{12V}{2\Omega} = 6 \text{ Ampere}$$

I_L is also flows through R_{th} .


Consider a fig -:-

Circuit (a) is

to be thevenized.

Here circuit with

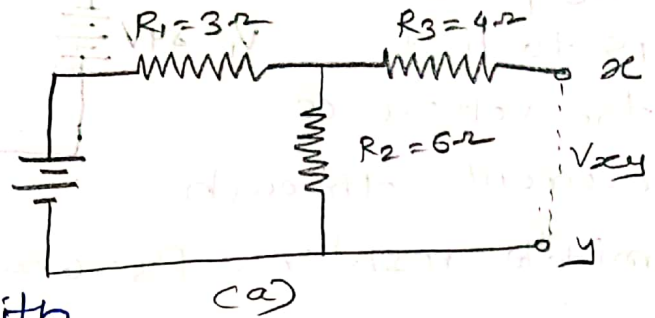$R_3 = 4\Omega$ in series with terminal x . @ Voltage V_{xy} is still 24V.




(b) But here R_3 does not change value of V_{xy} .

Resistance of R_{xy} is

~~$$R_{xy} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \times 6}{3 + 6}$$~~

~~$$R_{xy} = 6\Omega$$~~

~~$$R_{th} = R_{xy} + R_3 = 6\Omega$$~~

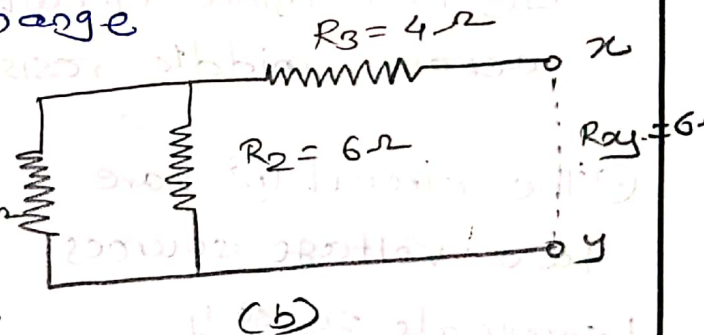

Here R_1 & R_2 are in parallel combination so they give combined resistance,


$$= \frac{R_1 R_2}{R_1 + R_2} = \frac{18}{9} = 2\Omega$$

& this resistance in series with $R_3 = 4\Omega$

$$\therefore R_{th} = 2 + 4 = 6\Omega$$


(b) Resistance R_{xy} is 6Ω

(c) Thus, thevenin equivalent circuit consists of $V_{th} = 24V$ & $R_{th} = 6\Omega$.

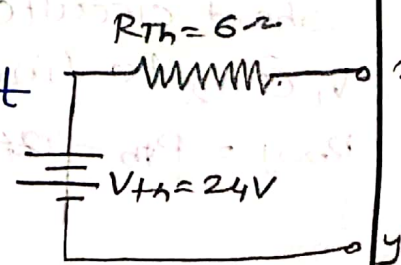

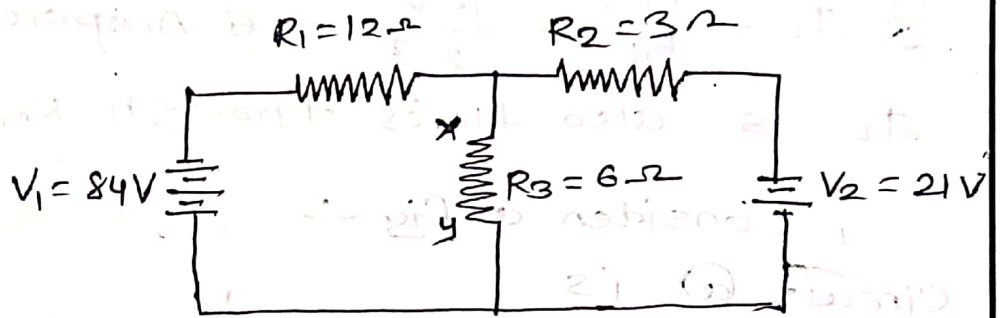Example II:-


The problem is to find the voltage & current through middle resistance $R_3 = 6\Omega$.



(a)

① Make the terminals x & y across R_3 (Fig @) fig @ is original circuit with terminals x & y across middle resistance R_3 .

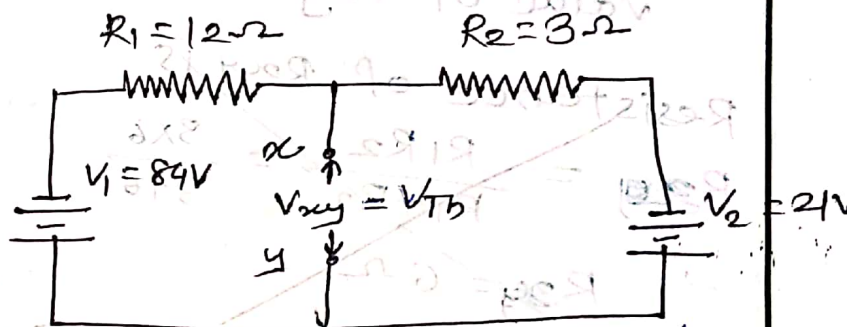② The circuit (b) have two voltage sources terminals x & y can be therezized




using formulae for V_{th} & R_{th} . Here disconnected R_3 to find V_{xy} .


$$V_{th} = V_{xy} = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} = \frac{(-84)3 + (-21)(12)}{12 + 3} = \frac{-504}{15} = -33.6V$$

$$\& R_{th} = R_{xy} = \frac{R_1 R_2}{R_1 + R_2} = \frac{36}{15} = 2.4\Omega$$

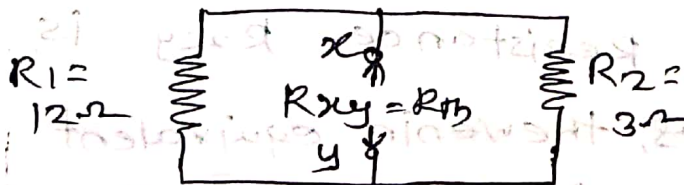③ circuit (c) is short circuited V_1 & V_2 to find $R_{xy} = R_{th} = 2.4\Omega$



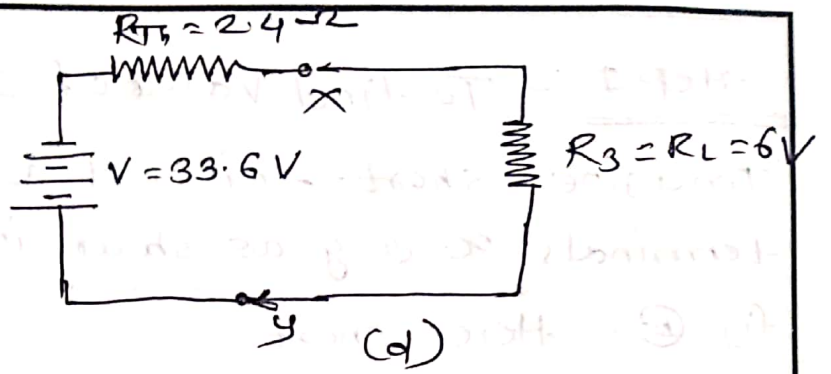④ fig. (d) is
 thevenin equivalent
 with $R_3 (= R_L)$
 reconnected to
 terminals x & y.




$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{33.6}{2.4 + 6} = \frac{33.6}{8.4} = \underline{4 \text{ Ampere}}$$

$$\& V_L = 6 \times 4 = \underline{24V}$$


* Norton's Theorem:-

Norton theorem is used to simplify a network in terms of current instead of voltages. It states that "the entire network connected to any two terminals x & y can be replaced by a single current source I_N in parallel with single resistance R_N ".

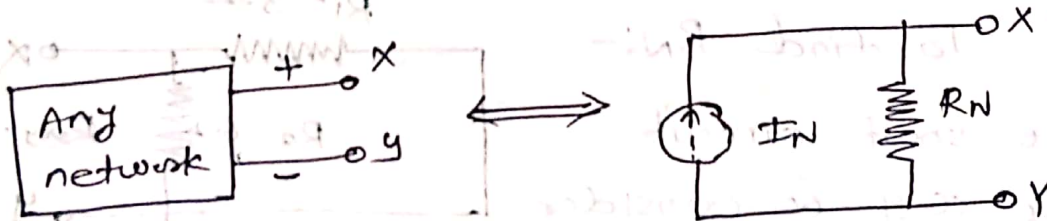

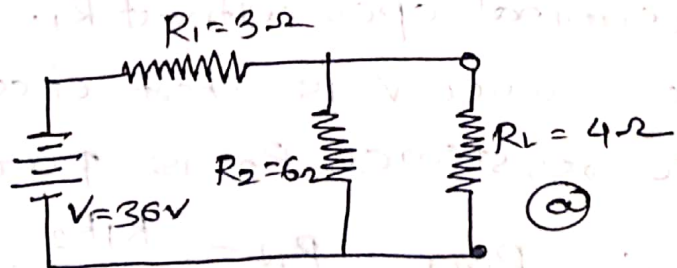Example I:-


① is original circuit. Let us calculate current I_L through load resistance $R_L = 4 \Omega$ as shown in fig ①



Step I :- To find value of I_N .

Imagine short-circuit across terminals x & y as shown in

fig (b). Here short

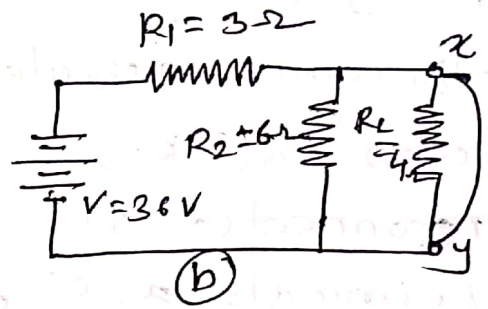


circuit R_L & also R_2 due to

R_2 & R_L are parallel. Then only resistance

in circuit is $R_1 = 3\Omega$ in series with $V = 36V$ as shown in fig (c).

The short circuit current

$$I_N = \frac{V}{R_1} = \frac{36}{3}$$

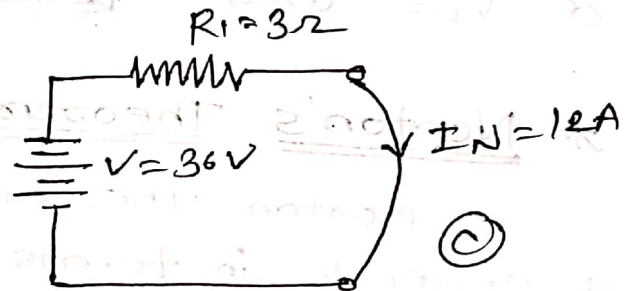


$$\therefore I_N = 12A$$

This $I_N = 12A$ is total current available from current source in Norton equivalent circuit shown in fig (d).

Step II :- To find R_N :-

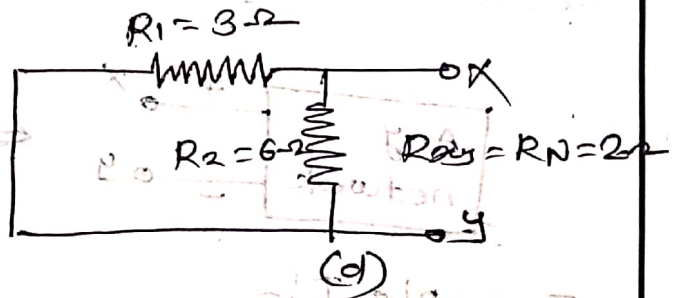Remove short circuit across x & y & consider terminal open without R_L .




Now source V is short circuited shown in fig (d).

So resistance R_2 is parallel to R_1 .


$$\therefore R_{xy} = R_N = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{6 + 3} = \underline{\underline{2\Omega}}$$

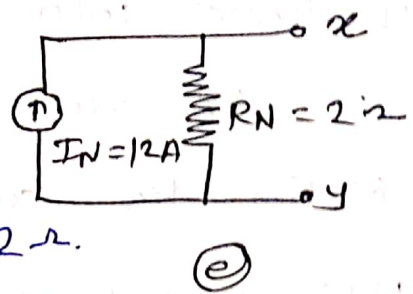Step III :- Draw a Norton equivalent circuit as shown in fig (c). It consists of current source $I_N = 12A$ & $R_N = 2\Omega$.



Step IV :- To calculate I_L :-

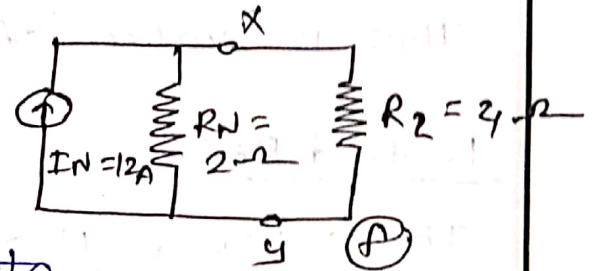
Reconnect $R_L = 4\Omega$ between x & y as shown in fig (d). Current source still deliver $12A$; but current divides into two branches of $R_N = 2\Omega$ & $R_L = 4\Omega$. Current through load resistance R_L is equal to



$$I_L = I_N \times \frac{R_N}{R_N + R_L} = 12 \times \frac{2}{2+4} = \underline{4A}$$

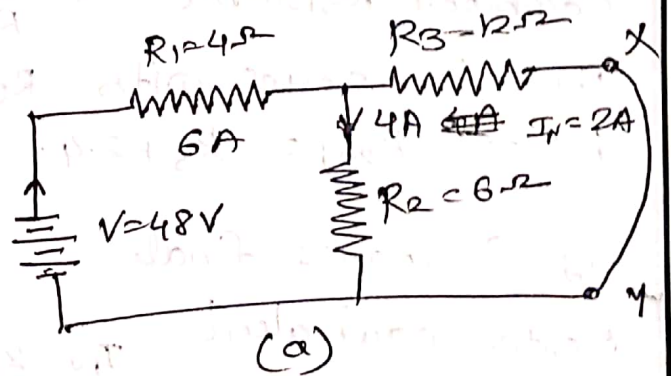Example II :-

In fig (a), $I_N = 2A$ is a branch current. I_N is through short-circuited terminals x, y



& R_3 .

To calculate I_N :- The parallel combination of R_3 & R_2 is equal to $\frac{R_2 R_3}{R_2 + R_3} = \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4\Omega$

Hence total resistance is $R_1 + \frac{R_2 R_3}{R_2 + R_3} = 4 + 4 = 8\Omega$

Hence total current from the source is $\frac{V}{R} = \frac{48}{8} = \underline{6A}$

It divides into $I \times \frac{R_2}{R_2 + R_3} = 6 \times \frac{12}{6+12} = \underline{4A}$

\therefore 4A current flows through R_3 .


& for R_3 , current is $I \times \frac{R_2}{R_3 + R_2} = 6 \times \frac{6}{6+12} = \underline{2A}$

This current of 2A flowing through R_3 flows through short circuited terminals x & y .

This is value of $I_N = 2A$.

To find R_N :

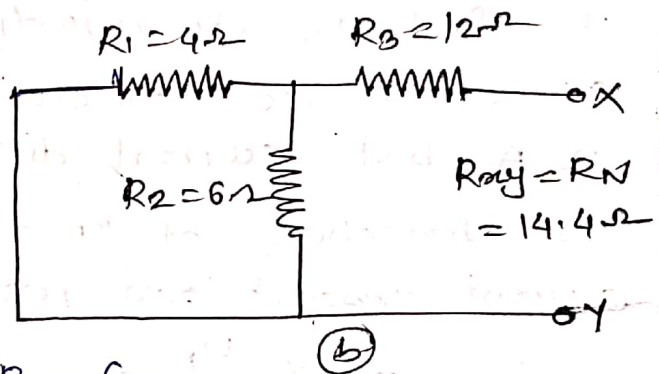The source v is short circuited in Fig (b). Also short circuit removed from x & y . Here,



$R_1 = 4\Omega$ is parallel with $R_2 = 6\Omega$


Combined resistance is $\frac{R_1 R_2}{R_1 + R_2} = \frac{4 \times 6}{4 + 6} = \underline{2.4\Omega}$

This is series with $R_3 = 12\Omega$.

Hence $R_{xy} = R_3 + 2.4 = 12 + 2.4 = \underline{14.4\Omega} = \underline{R_N}$

Fig (c) shows final

Norton equivalent circuit

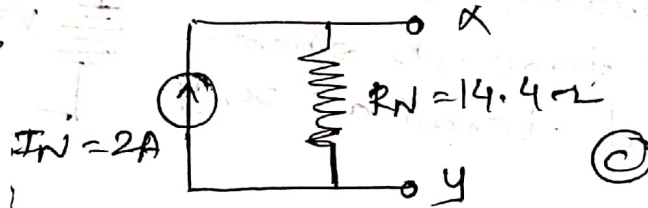

* Equivalence between Thevenin Theorem & Norton theorem:-

Thevenin theorem says that any network can be replaced by voltage source & a series resistance, while Norton's theorem states that the same network can

be replaced by current source & shunt resistance.
 It is possible to convert a Thevenin form to a Norton theorem & vice-versa.

The conversion formulae are: -



① Thevenin from Norton :-

$$R_{Th} = R_N \quad \& \quad V_{Th} = I_N \times R_N$$

② Norton from Thevenin :-

$$R_N = R_{Th} \quad \& \quad I_N = \frac{V_{Th}}{R_{Th}}$$

Example:- \uparrow

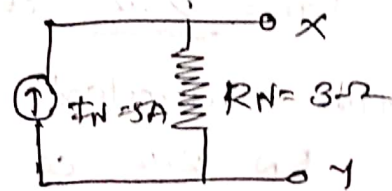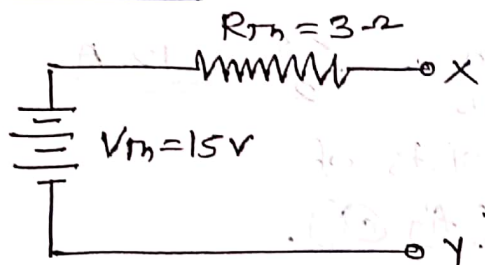




Ⓐ Thevenin equivalent circuit

Ⓑ corresponding Norton equivalent circuit

$$R_{Th} = R_N = \underline{3 \Omega}$$

$$V_{Th} = 15V \Rightarrow I_N = \frac{V_{Th}}{R_{Th}} = \frac{15}{3} = \underline{5A}$$

Example of Thevenin - Norton Conversion:

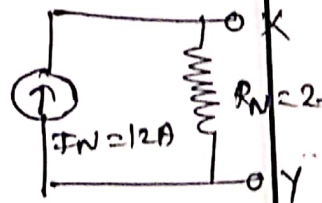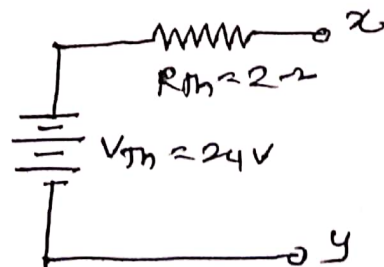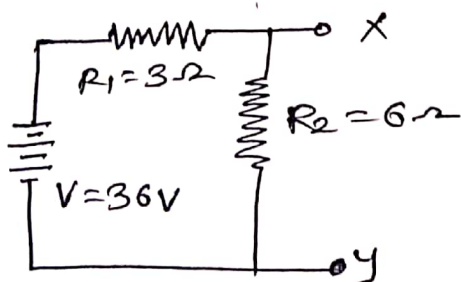

Ⓐ original circuit

Ⓑ Thevenin equivalent

Ⓒ Norton equivalent

Here in fig (a), voltage across R_2 is same as open voltage across terminals a & b.

Using voltage divider formula,

$$V_{ab} = V_{Th} = \frac{R_2}{R_1 + R_2} \times V = \frac{6}{3 + 6} \times 36$$

$$\therefore \underline{V_{Th} = 24V}$$

$$\& R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = \underline{2\Omega}$$



Therefore equivalent circuit consists of

$$V_{Th} = 24V \& R_{Th} = 2\Omega \text{ (fig (b))}$$

$$R_N = R_{Th} = \underline{2\Omega} \& I_N = \frac{V_{Th}}{R_{Th}} = \frac{24}{2} = \underline{12A}$$

Norton equivalent circuit consists of
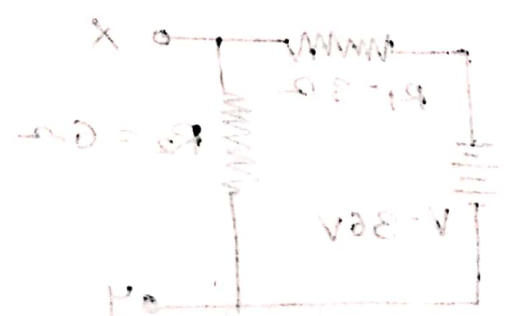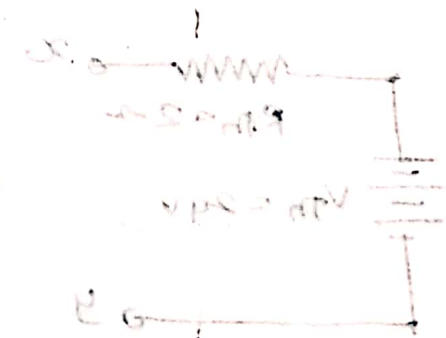
$$R_N = 2\Omega \& I_N = 12A \text{ (fig (c))}$$



load resistor

Thevenin circuit

Norton circuit